

OPERATING INSTRUCTIONS FOR ANDERSON'S BRIDGE

OBJECT:

To measure self inductance of a coil using Anderson's Bridge.

APPARATUS:

Anderson's Bridge has been designed on a training board New Tech Type NTI – 117. It consists three fixed resistances R_1 , R_2 , R_3 . R_1 is connected in between A and B. R_2 is connected in between B and C. Thus R_1 and R_2 form two ratio arms, R_3 is connected in between A and D and a variable resistance R_4 is connected in unknown arm C and D. The inductance (L) to be measured is also connected in the same arm. Thus R_4 and L are in series. A set of seven capacitors $C = C_1, C_2, C_3, C_4, C_5, C_6, C_7$ and resistance r in two steps of (i) $\times 100\Omega$ upto $1K\Omega$ (ii) $\times 1K\Omega$ upto $10 K\Omega$ are provided on the board. Fixed frequency oscillator is connected in the bridge two terminal provided for this. A headphone or galvanometer fitted with diode is joined in between two terminals marked for this purpose. Three inductances L_1 , L_2 and L_3 are also provided on the board. L_1 is between first and second terminal, L_2 is between second and third terminal, L_3 is in between third and fourth terminal.

THEORY:

When Anderson Bridge is balanced in the sound in head phone or deflection in galvanometer fitted with diode is minimum. The potential at E & F is same then:

$$\therefore \frac{P}{Q} = \frac{R}{S}$$

$$\therefore \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

And if $P = Q$ or $R_1 = R_2$

$$L = CR_3 (R_2 + 2r) \dots\dots\dots (1)$$

PROCEDURE:

- (1) Connect one self inductance say L2 (second and third terminals) to the sockets provided across the symbol of the Coil in the bridge circuit.
- (2) Connect a leclanche cell or lead accumulator in place of oscillator and Galvanometer at place of head phone. Adjust R4 so that Zero deflection is obtained in Galvanometer keeping r at 0 resistance.
- (3) Now disconnect leclanche cell and at its place connect fixed frequency oscillator. Head phone or Galvanometer fitted with diode is connected at its proper place.
- (4) Set suitable value of C and by changing r obtain minimum sound in head phone or minimum deflection in Galvanometer. Record the value of C and r in O.T.
- (5) Changing value of C repeat step (4) a number of times. Record the value of C and r in O.T.
- (6) Calculate L using formula (1) given in theory.

OBSERVATIONS : Given Values :

$$R_1 = R_2 = R_3 = 1K\Omega$$

$$C_1 = \dots\dots \mu F, C_2 = \dots\dots \mu F, C_3 = \dots\dots \mu F$$

$$C_4 = \dots\dots \mu F, C_5 = \dots\dots \mu F, C_6 = \dots\dots \mu F \text{ and } C_7 = \dots\dots \mu F$$

$$L_1 = \dots\dots \text{ mH}, L_2 = \dots\dots \text{ mH}, L_3 = \dots\dots \text{ mH}$$

S. No.	Value of C μF	Resistance r Ohms	Inductance L mH
1			
2			
3			

Mean Value of L = mH

CALCULATIONS:

$$L = CR_3 (R_2 + 2r) \text{ Henry}$$
$$= CR_3 (R_2 + 2r) \times 10^3 \text{ mH}$$

RESULT:

Inductance of the given:

Coil = mH

Standard value = mH

PRECAUTIONS:

- (1) Initially the output of frequency oscillator should be kept low and near null point it should be increased.
- (2) If head phone is used these should be silence in the neighbouring.
- (3) For greater sensitivity of the bridge resistances in the four arms should be nearly same.
- (4) Plug type Resistance box or P.O. box should not be used.
- (5) For obtaining balance point $L > CR_2R_3$.
- (6) For inductance L_1 is of low value C_1, C_2, C_3 capacitors should be used. For inductance L_2 is medium value C_3, C_4, C_5 . Capacitors should be used and for L_3 Capacitors C_5, C_6, C_7 should be used to get null point and better results.

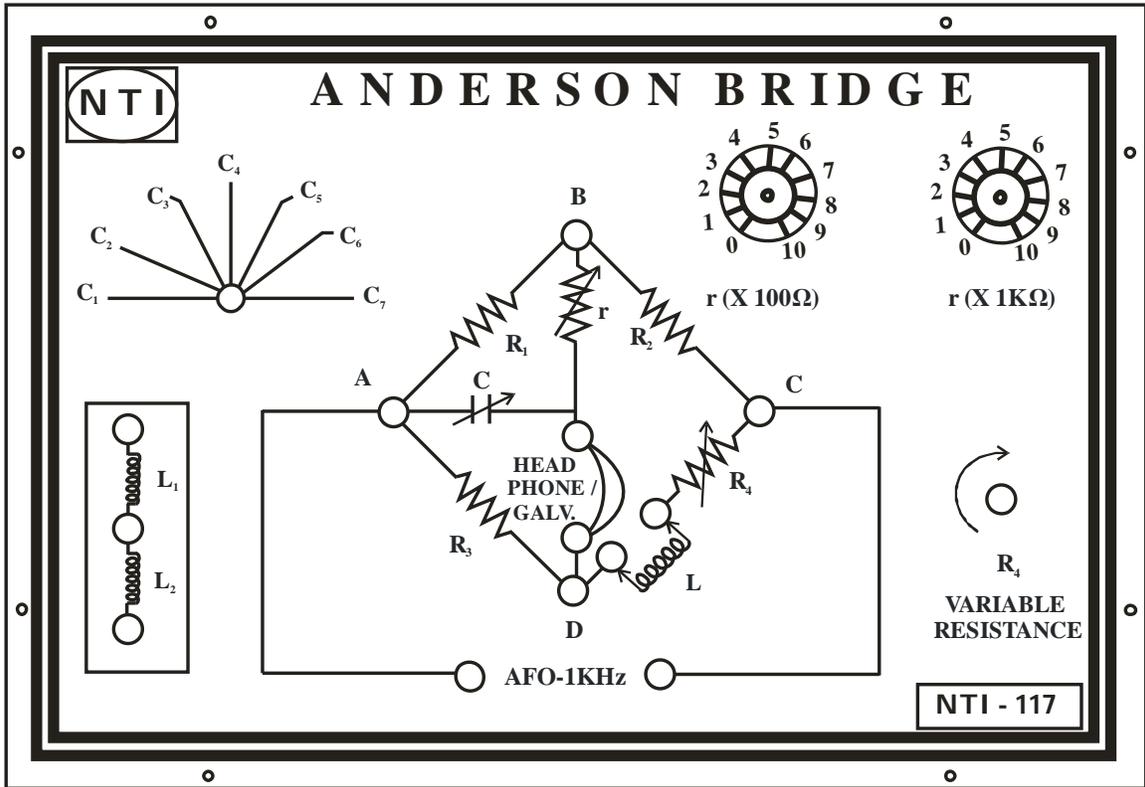


Fig. (1) Panel Diagram
